

1.1. Complete the SST basing on time diagram. If the table is not solvable, mark the placement of the proper borders (1.5 pt).

1.2. For the SST given below provide:

a) the solvable table (1 pt).

b) definitions of functions describing the circuit in the canonical form (0.5 pt).

1.3. For the function definitions given below, provide the minimal expressions for implementation: a) for Z using NOR gates (1 pt), b) for W using ~or flip-flop (1 pt).

$Z = \sum_{(0,1,2,4,8,9,10,11)} m_{abc}$ $W = \sum_{(1,6,9,10,11,14)} m_{abc}$

$Z = \omega\bar{b} + \bar{\omega}a + \bar{z}b\bar{a}$ $W = \bar{u} + b + \bar{a}$

$$S_0 = \bar{b}b\bar{a}$$

$$\bar{S}_0 = \omega + b + \bar{a}$$

2.1. For the circuit described by the timing chart provide the primitive flow map (1.0 pts).

2.2. For the primitive flow map given, list equivalent and pseudo-equivalent states, and conduct the 1st reduction stage (1.5 pts).

2.3. For the flow table given conduct the reduction of compatible states (2nd reduction stage) for Mealy machine, obtaining the minimal number of rows. Draw the merger diagram (0.5 pts), present the symbolic flow map, encoded binary internal state map (eliminate possible races), and output map (1.0 pts).

2.4. Analyse the circuit described by the flow map with respect to racing races.

2.5. Huffman's method

3.1. Design the graph for the sequential circuit detecting that the sum of bits in 2-bit words given to the serial input X equals to 1. It should be signalled by setting the output W=1 for the single clock period (1.5 pt).



3.2. Design the parallel counter with a programming input p and counting codes as given below. Apply synchronous illegal state recovery. Provide the binary program map (2 pt).

Counting codes:

11 → 10 → 00

01 → 10 → 11

3 → 2 → 0

1 → 2 → 3

Program map:

$Q_1^*Q_0^*$	0	1	W
00	11	01	00
01	11	10	01
11	10	01	11
10	00	11	10

3.3. For the circuit described by the program map present the equations for the implementation for T flip-flops (1.5 pt).

Program map:

$Q_1^*Q_0^*$	0	1
00	10	00
01	11	10
11	11	01
10	11	00

Equations:

$$T_1 = \bar{Q}_1\bar{p} + \bar{Q}_1Q_0 + Q_1\bar{p}$$

$$T_0 = \bar{Q}_1Q_0p + Q_1\bar{Q}_0\bar{p}$$

4. Design microprogrammable circuit working according to the presented graph. The solution should be as optimal as possible in respect to the memory size. Provide the solution in the form of:

a) microprogram proper for the given diagram (2.5 pt).

b) diagram proper for the given microprogram (2.5 pt).

Microprogram:

$Q_1^*Q_0^*$	Q_1^{**}	Q_0^{**}	Z_1	Z_0
00	0	0	0	0
01	1	1	0	0
11	1	1	1	0
10	1	1	1	1

Diagram: